

Comparators connected to voltages with $V > V_i$ produce one polarity,
All connected to $V < V_i$ produce the opposite polarity.
Combinational logic is then used to determine the value of the input
voltage from this pattern.

– a parallel or flash ADC

Go fast converter (ns)
Accurate and expensive

