

Built V_{ref}
divided it

Comparators

Voltage changes $\Rightarrow$ bit change (a b c d)

Converted a b c d to a binary count

What have we left off?

Want to Read binary count & don't want it
changing when we read it