

Do we always get a nice Sine Wave?

No, need to balance components to avoid

The flat top: 

The banana: 

The ex-oscillator



The won't oscillate



Tips on getting the oscillator to actually oscillate available in the TI op amp book (in supplemental materials) under oscillators, OR from Lise and the lab assistants!